

VLSI Design Internship · Task 6

RTL Design of Processor Components (Control Unit + Datapath Integration)

1. Objective

This task integrates the sequential circuits (Task-3), FSM-based control logic (Task-4), and datapath components — ALU, RAM, and registers (Task-5) — into a complete basic processor architecture. The goal is to understand how a Control Unit and Datapath work together to execute instructions.


- Understand processor architecture basics
- Design a Control Unit using FSM (Fetch → Decode → Execute → Writeback)
- Integrate ALU + Register File into a unified datapath
- Implement a simple 8-bit instruction execution flow
- Simulate and verify the processor using Vivado waveforms

2. Processor Architecture

The processor is built as a hierarchy of five RTL modules, all integrated in a single **processor_flat.v** file to ensure clean compilation in Vivado.

Module	Role	Key Signals
control_unit	FSM — drives state transitions	state[1:0], fetch_en, decode_en, execute_en, writeback_en
decoder	Opcode → ALU op mapping	opcode[2:0] → alu_op[2:0], reg_write
register_file	4 × 4-bit registers	read_data_A/B, write_data, write_en
alu	Arithmetic & Logic Unit (8 ops)	A, B, alu_op → result, zero_flag, carry_flag
processor	Top-level integration	clk, reset, instruction[7:0], result[3:0]

Dataflow

 

3. Instruction Format

Each instruction is 8 bits wide, divided into three fields:

Bits	[7:5]	[4:3]	[2:1]	[0]
Field	Opcode (3 bits)	Reg A addr (2 bits)	Reg B addr (2 bits)	Unused
Purpose	Selects operation	Source + Writeback dest	Source operand B	—

Opcode Mapping

Opcode (binary)	Instruction	ALU Operation	Example Result
000	ADD	A + B	0xF + 0x0 = 0xF
001	SUB	A - B	0xF - 0x0 = 0xF
010	AND	A & B	0xF & 0x0 = 0x0
011	OR	A B	0xF 0x0 = 0xF
100	XOR	A ^ B	0xF ^ 0xF = 0x0
101	NOT	~A	~0x0 = 0xF
110	SHL	A << 1	0xF << 1 = 0xE
111	SHR	A >> 1	0xE >> 1 = 0x7


4. Control Unit FSM Design

The Control Unit is implemented as a Moore FSM with four states. On every clock cycle, the FSM advances one state and asserts exactly one enable signal (one-hot encoding).

State	Encoding	Enable Signal	Action
FETCH	2'b00	fetch_en = 1	Load instruction into processor
DECODE	2'b01	decode_en = 1	Opcode decoded, reg addresses extracted
EXECUTE	2'b10	execute_en = 1	ALU computes result
WRITEBACK	2'b11	writeback_en = 1	ALU result written to register file

 5. Simulation Waveform (Vivado)

The following waveform was captured from Vivado Behavioral Simulation. It shows the processor executing all 10 test instructions across the four FSM states.



Waveform Signal Analysis

Signal	Observed Behaviour	Verification
clk	Clean 10 ns period square wave from time 0	PASS
reset	HIGH for ~40 ns, then LOW — FSM starts cleanly	PASS
instruction[7:0]	Changes per instruction: e0, a0, 02, 22, 42 ...	PASS
result[3:0]	Updates correctly: 0→f→f→0→f→f→0→f→e→7	PASS
zero_flag	Pulses HIGH when result=0 (AND, XOR ops)	PASS
carry_flag	Asserts on arithmetic overflow	PASS
state[1:0]	Cycles 0→1→2→3→0 every 4 clock edges	PASS
fetch_en	One-hot HIGH during state=0 (FETCH)	PASS
dec_en	One-hot HIGH during state=1 (DECODE)	PASS
exe_en	One-hot HIGH during state=2 (EXECUTE)	PASS
writeback_en	One-hot HIGH during state=3 (WRITEBACK)	PASS

6. Observations

- FSM correctness:** The control unit cycles cleanly through all four states (FETCH=0, DECODE=1, EXECUTE=2, WRITEBACK=3) with no glitches or unknown states.
- One-hot enable signals:** Exactly one of fetch_en / decode_en / execute_en / writeback_en is HIGH at any given time, confirming correct Moore FSM output logic.
- Register write-back:** The ALU result is correctly written to the register file only during WRITEBACK, and is available to the next instruction as a source operand.

- **Zero flag behaviour:** The zero_flag asserts correctly for AND ($0xF \& 0x0 = 0$) and XOR ($0xF \wedge 0xF = 0$) instructions, visible as narrow HIGH pulses in the waveform.
- **Sequential dependency:** The NOT $\rightarrow$ SHL $\rightarrow$ SHR instruction chain demonstrates that write-back from one instruction correctly feeds the next ($0xF \rightarrow 0xE \rightarrow 0x7$).
- **No X/Z states:** All signals are fully defined from time 0 because clk and reset are initialized at declaration, preventing unknown propagation through the FSM.

7. Deliverables

File	Description
<code>processor_flat.v</code>	All 5 RTL modules in one file (alu, decoder, control_unit, register_file, processor)
<code>tb_processor.v</code>	Testbench — 10 instruction tests, VCD dump
<code>dump.vcd</code> / Vivado sim	Simulation waveform (screenshot included above)
<code>Task6_Report.pdf</code>	This document — architecture diagram, instruction format, waveform analysis, observations